

```

/*****
* Date: Aug. 16, 2006
* File: Mux_16_to_1.v (440 Examples)
*
* Structural of a 16 to 1 MUX (Sixteen 1-bit inputs) that is built
* using two 8-to-1 muxes that feed a 2-to-1 mux.
*
* Note the use of a continuous assignment statement for implementing
* the combinational logic, avoiding the necessity of a "register"
* data type for output Y.
*****/

//*****
module mux_16to1(Y, In, sel);

//*****

    output        Y;
    input [15:0] In;
    input [3:0]   sel;
    wire          lo8, hi8, out1;

    // Instantiate the 8-to-1 muxes and the 2-to-1 mux
    mux_8to1 mux_lo (lo8, In[7:0], sel[2:0]);
    mux_8to1 mux_hi (hi8, In[15:8], sel[2:0]);
    mux_2to1 mux_out (out1, lo8, hi8, sel[3]);

    // equate the wire out of the 2-to-1 with
    // the actual output (Y) of the 16-to-1 mux
    assign Y = out1;

endmodule

```