

Using Verilog for Testbenches

Design of Digital Circuits 2014

Srdjan Capkun

Frank K. Gürkaynak

http://www.syssec.ethz.ch/education/Digitaltechnik_14

What Will We Learn?

- How to simulate your circuit
- Applying inputs
- Seeing if the circuit does the correct thing

How Do You Know That A Circuit Works?

- **You have written the Verilog code of a circuit**
 - Does it work correctly?
 - Even if the syntax is correct, it might do what you want?
 - What exactly it is that you want anyway?
- **Trial and error can be costly**
 - You need to 'test' your circuit in advance
- **In modern digital designs, functional verification is the most time consuming design stage.**

The Idea Behind A Testbench

- **Using a computer simulator to test your circuit**
 - You instantiate your design
 - Supply the circuit with some inputs
 - See what it does
 - Does it return the “correct” outputs?

Testbenches

- HDL code written to test another HDL module, the *device under test* (dut), also called the *unit under test* (uut)
- Not synthesizable
- Types of testbenches:
 - Simple testbench
 - Self-checking testbench
 - Self-checking testbench with testvectors

Example

- Write Verilog code to implement the following function in hardware:

$$y = (\overline{b} \cdot \overline{c}) + (a \cdot \overline{b})$$

- Name the module sillyfunction

Example

- Write Verilog code to implement the following function in hardware:

$$y = (\overline{b} \cdot \overline{c}) + (a \cdot \overline{b})$$

- Name the module sillyfunction

```
module sillyfunction(input  a, b, c,  
                    output y);  
  
    assign y = ~b & ~c | a & ~b;  
endmodule
```

Simple Testbench

```
module testbench1(); // Testbench has no inputs, outputs
    reg  a, b, c;      // Will be assigned in initial block
    wire y;

    // instantiate device under test
    sillyfunction dut (.a(a), .b(b), .c(c), .y(y) );d

    // apply inputs one at a time
    initial begin          // sequential block
        a = 0; b = 0; c = 0; #10; // apply inputs, wait 10ns
        c = 1; #10;           // apply inputs, wait 10ns
        b = 1; c = 0; #10;     // etc .. etc..
        c = 1; #10;
        a = 1; b = 0; c = 0; #10;
    end
endmodule
```


Simple Testbench

- Simple testbench instantiates the design under test
- It applies a series of inputs
- The outputs have to be observed and compared using a simulator program.
 - This type of testbench does not help with the outputs
- **initial** statement is similar to **always**, it just starts once at the beginning, and does not repeat.
- The statements have to be blocking.

Self-checking Testbench

```
module testbench2();
  reg  a, b, c;
  wire y;

  // instantiate device under test
  sillyfunction dut(.a(a), .b(b), .c(c), .y(y));

  // apply inputs one at a time
  initial begin
    a = 0; b = 0; c = 0; #10; // apply input, wait
    if (y !== 1) $display("000 failed."); // check
    c = 1; #10; // apply input, wait
    if (y !== 0) $display("001 failed."); // check
    b = 1; c = 0; #10; // etc.. etc..
    if (y !== 0) $display("010 failed."); // check
  end
endmodule
```


Self-checking Testbench

- Better than simple testbench
- This testbench also includes a statement to check the current state
- `$display` will write a message in the simulator
- This is a lot of work
 - Imagine a 32-bit processor executing a program (thousands of clock cycles)
- You make the same amount of mistakes when writing testbenches as you do writing actual code

Testbench with Testvectors

- **The more elaborate testbench**
- **Write testvector file: inputs and expected outputs**
 - Usually can use a high-level model (golden model) to produce the 'correct' input output vectors
- **Testbench:**
 - Generate clock for assigning inputs, reading outputs
 - Read testvectors file into array
 - Assign inputs, get expected outputs from DUT
 - Compare outputs to expected outputs and report errors

Testbench with Testvectors

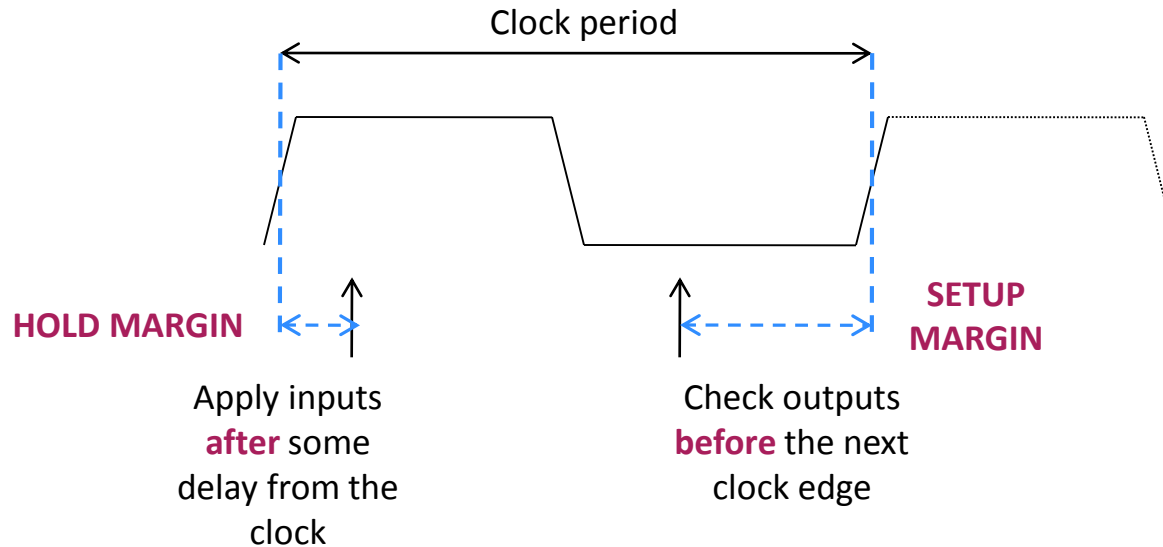

- **A testbench clock is used to synchronize I/O**
 - The same clock can be used for the DUT clock
- **Inputs are applied following a hold margin**
- **Outputs are sampled before the next clock edge**
 - The example in book uses the falling clock edge to sample

Testvectors File

- We need to generate a testvector file (somehow)
- File: `example.tv` – contains vectors of `abc_yexpected`

`000_1`

`001_0`

`010_0`

`011_0`

`100_1`

`101_1`

`110_0`

`111_0`

Testbench: 1. Generate Clock

```
module testbench3();
    reg          clk, reset;    // clock and reset are internal
    reg          a, b, c, yexpected; // values from testvectors
    wire         y;             // output of circuit
    reg [31:0] vectornum, errors; // bookkeeping variables
    reg [3:0] testvectors[10000:0]; // array of testvectors

    // instantiate device under test
    sillyfunction dut(.a(a), .b(b), .c(c), .y(y) );

    // generate clock
    always        // no sensitivity list, so it always executes
    begin
        clk = 1; #5; clk = 0; #5;    // 10ns period
    end
```

2. Read Testvectors into Array

```
// at start of test, load vectors
// and pulse reset

initial                // Will execute at the beginning once
begin
    $readmemb("example.tv", testvectors); // Read vectors
    vectornum = 0; errors = 0;              // Initialize
    reset = 1; #27; reset = 0;             // Apply reset wait
end

// Note: $readmemb reads testvector files written in
// hexadecimal
```


3. Assign Inputs and Expected Outputs

```
// apply test vectors on rising edge of clk
always @(posedge clk)
  begin
    #1; {a, b, c, yexpected} = testvectors[vectornum];
  end
```

- Apply inputs with some delay (1ns) AFTER clock
- This is important
 - Inputs should not change at the same time with clock
- Ideal circuits (HDL code) are immune, but real circuits (netlists) may suffer from hold violations.

4. Compare Outputs with Expected Outputs

```
// check results on falling edge of clk
always @(negedge clk)
  if (~reset)                      // skip during reset
    begin
      if (y !== yexpected)
        begin
          $display("Error: inputs = %b", {a, b, c});
          $display("  outputs = %b (%b exp)", y, yexpected);
          errors = errors + 1;
        end
    end
// Note: to print in hexadecimal, use %h. For example,
//       $display("Error: inputs = %h", {a, b, c});
```

4. Compare Outputs with Expected Outputs

```
// increment array index and read next testvector
vectornum = vectornum + 1;
if (testvectors[vectornum] === 4'bx)
begin
    $display("%d tests completed with %d errors",
            vectornum, errors);
    $finish;                // End simulation
end
end
endmodule

// Note: === and !== can compare values that are
// x or z.
```

Golden Models

- **A golden model represents the ideal behavior of your circuit.**
 - Still it has to be developed
 - It is difficult to get it right (bugs in the golden model!)
 - Can be done in C, Perl, Python, Matlab or even in Verilog
- **The behavior of the circuit is compared against this golden model.**
 - Allows automated systems (very important)

Why is Verification difficult?

■ How long would it take to test a 32-bit adder?

- In such an adder there are 64 inputs = 2^{64} possible inputs
- That makes around 1.85×10^{19} possibilities
- If you test one input in 1ns, you can test 10^9 inputs per second
 - or 8.64×10^{14} inputs per day
 - or 3.15×10^{17} inputs per year
- we would still need **58.5 years** to test all possibilities

■ Brute force testing is not feasible for all circuits, we need alternatives

- Formal verification methods
- Choosing 'critical cases'
- Not an easy task

What did we learn?

- **Verilog has other uses than modeling hardware**
 - It can be used for creating testbenches
- **Three main classes of testbenches**
 - Applying only inputs, manual observation (**not a good idea**)
 - Applying and checking results with inline code (**cumbersome**)
 - Using testvector files (**good for automatization**)