```
/************************
* Date: Aug. 28, 1999
* File: Decoder 3 to 8.v (440 Examples)
* Module of a 3 to 8 Decoder with an active high enable input and
* and active low outputs. This model uses a trinary continuous
* assignment statement for the combinational logic
*****************************
//***********************
 module decoder_3to8(Y7, Y6, Y5, Y4, Y3, Y2, Y1, Y0, A, B, C, en);
//**********************************
    output Y7, Y6, Y5, Y4, Y3, Y2, Y1, Y0;
    input A, B, C;
    input en;
    assign \{Y7, Y6, Y5, Y4, Y3, Y2, Y1, Y0\} = (\{en, A, B, C\} == 4'b1000) ? 8'b1111_1110 :
                                   \{en,A,B,C\} == 4'b1001\} ? 8'b1111_1101 :
                                  (\{en,A,B,C\} == 4'b1010) ? 8'b1111_1011 :
                                  \{en,A,B,C\} == 4'b1011\} ? 8'b1111_0111 :
                                  \{en,A,B,C\} == 4'b1100\}? 8'b1110_1111:
                                  \{en,A,B,C\} == 4'b1101\} ? 8'b1101 1111 :
                                  \{en,A,B,C\} == 4'b1110\} ? 8'b1011_1111 :
                                  \{en,A,B,C\} == 4'b1111\} ? 8'b0111_1111 :
                                                          8'b1111_1111;
```

endmodule